



APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

LOGIC CIRCUIT DESIGN (ECT-203)

MODULE 3 NOTES

PREPARED BY : JIBIN EP, ASSISTANT PROFESSOR, EKC TC MANJERI

INDEX

SL NO	TOPIC	SLIDE LINK	VIDEO LINK
1	Introduction To Combinational Circuits	INTRODUCTION TO COMBINATIONAL CIRCUITS	https://youtu.be/gvTM4oGD_XU
2	Design Of Adders (Half Adder And Full Adder)	DESIGN OF ADDERS (HALF ADDER AND FULL ADDER)	https://youtu.be/gvTM4oGD_XU
3	Design Of Subtractors (Half Subtractor And Full Subtractor)	DESIGN OF SUBTRACTORS (HALF SUBTRACTOR AND FULL SUBTRACTOR)	https://youtu.be/FOGczanvVEk
4	Multiplexer And Demultiplexer	MULTIPLEXER AND DEMULTIPLEXER	https://youtu.be/J8-fKhmlWuQ https://youtu.be/Tt_cZOn2YBA
5	Multiplexer And Demultiplexer (Numerical Problems)	MULTIPLEXER AND DEMULTIPLEXER (NUMERICAL PROBLEMS)	https://youtu.be/2p9Ex6YPBc4
6	Decoder And Encoder	DECODER AND ENCODER	https://youtu.be/Zxd-imLGIFc
7	Magnitude Comparator	MAGNITUDE COMPARATORS	https://youtu.be/7xHM5HeGCHQ
10	Binary Parallel Adder, Carry Look Ahead Adder & Bcd Adder	BINARY PARALLEL ADDER CARRY LOOK AHEAD ADDER BCD ADDER	https://youtu.be/8G29l4BFg_o https://youtu.be/hfbvmGZ79SA
10	Verilog Programming Part 2	Verilog Programming Part 2	https://youtu.be/ZgGDLuHmpOE

Module 3: Combinatorial and Arithmetic Circuits

Combinatorial Logic Systems - Comparators, Multiplexers, Demultiplexers, Encoder, Decoder. Half and Full Adders, Subtractors, Serial and Parallel Adders, BCD Adder. Modeling and simulation of combinatorial circuits with verilog codes at the gate level.

3	Combinatorial and Arithmetic Circuits	
3.1	Combinatorial Logic Systems - Comparators, Multiplexers, Demultiplexers	2
3.2	Encoder, Decoder, Half and Full Adders, Subtractors, Serial and Parallel Adders, BCD Adder	3
3.3	Gate level modelling combinatorial logic circuits in Verilog: half adder, full adder, mux, demux, decoder, encoder	3

MODULE 3 (TOPIC-1)

INTRODUCTION TO COMBINATIONAL CIRCUITS

https://youtu.be/gvTM4oGD_>



JIBIN EP, EKC TC MANJERI, 9633908979

5


Combinational Logic Circuits

- When Logic Gates are connected together to produce a specified output for certain specified combination of input variables, with no storage involved, the resulting circuit is called combinational logic circuit
- In Combinational Logic Circuits, the output variables are all time depends on combination of input variables
- A Combinational Circuit consist of Input variables, Logic Gates & Output Variables.
- The Logic Gates accepts signal from the input variable and generate output signals

JIBIN EP, EKC TC MANJERI, 9633908979

6

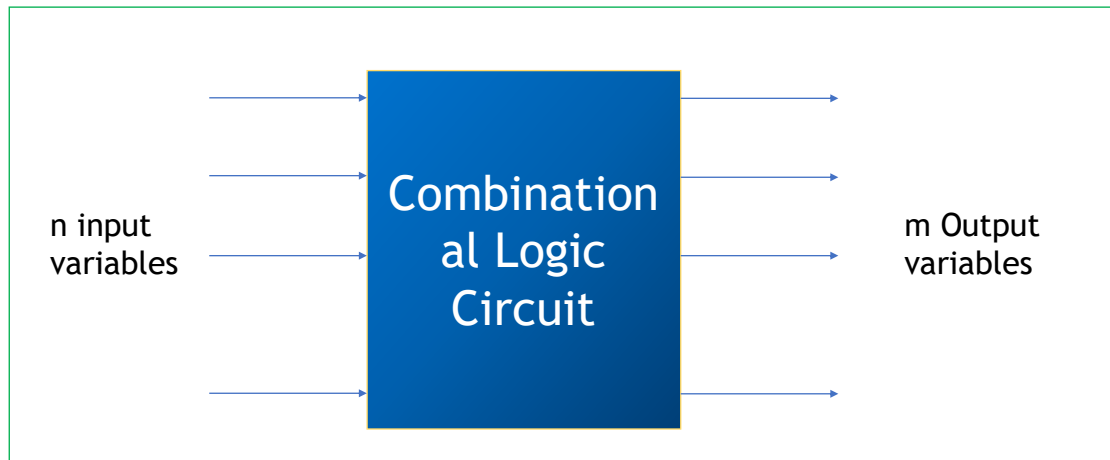
Block Diagram of Combinational Logic Circuit



JIBIN EP, EKC TC MANJERI, 9633908979

7

TYPES OF COMBINATIONAL CIRCUITS

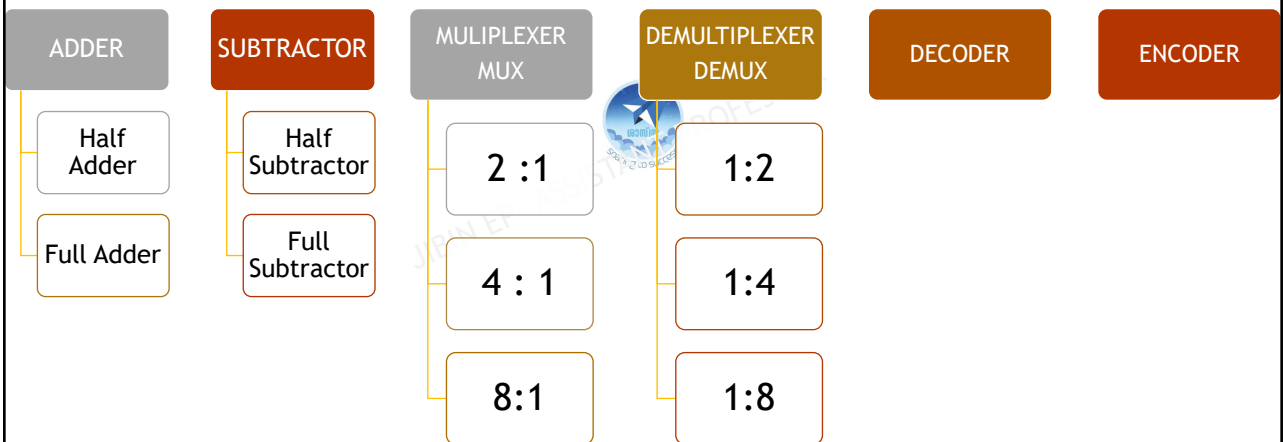

JIBIN EP, EKC TC MANJERI, 9633908979

8

Design Procedure

- 1 Problem Definition
- 2 Determination of input and output variables
- 3 Assigning letter symbols to input and output variables
- 4 Derivation of Truth Table
- 5 Obtain Simplified Boolean Expression
- 6 Obtain the Logic Diagram

JIBIN EP, EKC TC MANJERI, 9633908979

9

Example 1 :

Design a combinational Logic Circuit with three input variables that will produce a logic 1 output when more than one input variable are logic 1

TRUTH TABLE


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

BOOLEAN EXPRESSION

BC	00	01	11	10
A	0	0	1	0
0	0	0	1	0
1	0	1	1	1

$$Y = AC + BC + AB$$

LOGIC DIAGRAM

 

JIBIN EP, EKC TC MANJERI, 9633908979

10

Example 2 :

A Majority gate is digital circuit whose output is equal to 0 if majority of inputs are 1's . The output is 1 otherwise.
Using TT Find Boolean Function and Logic Diagram

TRUTH TABLE

BOOLEAN EXPRESSION

LOGIC DIAGRAM



JIBIN EP, EKC TC MANJERI, 9633908979

11

MODULE 3 (TOPIC-2)

DESIGN OF ADDERS (HALF ADDER AND FULL ADDER)

https://youtu.be/gvTM4oGD_XU  YouTube

JIBIN EP, EKC TC MANJERI, 9633908979

12

Design of Adders

$$0+0=0$$

$$0+1=1$$

$$1+0=1$$

$$1+1=10$$

(1+1= Sum 0,
Carry 1)

- The Simple addition consist of four possible elementary operations
- The First 3 Operations Produces Sum whose length is one digit
- Last Operation Performed sum in two digits. Higher Significant result is Called Carry & Lower Significant bit is Called Sum

JIBIN EP, EKC TC MANJERI, 9633908979

13

HALF ADDER

- Half adder is a combinational logic circuit with two inputs and two outputs.
- The half adder circuit is designed to add two single bit binary number A and B.
- It is the basic building block for addition of two **single** bit numbers. This circuit has two outputs **carry** and **sum**.



JIBIN EP, EKC TC MANJERI, 9633908979

14

HALF ADDER

0+0=0, 0+1=1
1+0=1, 1+1=0

TRUTH TABLE

Inputs		Outputs	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

BOOLEAN EXPRESSION

For Carry


A \ B	0	1
0	0	0
1	0	1

$$\text{Carry} = AB$$

For Sum

A \ B	0	1
0	0	1
1	1	0
 
$$\begin{aligned}\text{Sum} &= AB + \bar{A}B \\ &= A \oplus B\end{aligned}$$




JIBIN EP, EKC TC MANJERI, 9633908979

15

FULL ADDER

 - Full adder is developed to overcome the drawback of Half Adder circuit.
- It can add two one-bit numbers A and B, and C.
- The full adder is a three input and two output combinational circuit.



JIBIN EP, EKC TC MANJERI, 9633908979

16



FULL ADDER

0+0=0, 0+1=1
1+0=1, 1+1=0

TRUTH TABLE

Inputs			Outputs	
A	B	C _{in}	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

BOOLEAN EXPRESSION

  


JIBIN EP, EKC TC MANJERI, 9633908979

17

Reference : 3 Input XOR Gate

Inputs			outputs
W	X	Y	Q = A ⊕ B ⊕ C
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

$Sum = A \oplus B \oplus C_{in}$


JIBIN EP, EKC TC MANJERI, 9633908979

18

FULL ADDER

0+0=0, 0+1=1
1+0=1, 1+1=0

LOGIC DIAGRAM

 

$$\text{Sum} = A \oplus B \oplus C_{in}$$

$$\text{Carry} = AB + AC_{in} + BC_{in}$$

JIBIN EP, EKC TC MANJERI, 9633908979


19

FULL ADDER

0+0=0, 0+1=1
1+0=1, 1+1=0

LOGIC DIAGRAM

 Implementation of Full Adder Circuit using two Half Adders



JIBIN EP, EKC TC MANJERI, 9633908979

20

MODULE 3 (TOPIC-3)

DESIGN OF SUBTRACTORS (HALF SUBTRACTOR AND FULL SUBTRACTOR)

<https://youtu.be/FOGczanvVBk>



JIBIN EP, EKC TC MANJERI, 9633908979

21

Design of Subtractors

$$0-0=0$$

$$0-1=1 \text{ With Borrow } 1$$

$$1-0=1$$

$$1-1=0$$


- The Simple Subtraction consist of four possible elementary operations
- The First , 3rd and 4th Operations Produces Difference whose length is one digit. In these Operations, Each Subtrahend bit is subtracted from Minuend bit
- 2nd Operation the minuend bit is smaller than the subtrahend bit, Hence 1 is borrowed

JIBIN EP, EKC TC MANJERI, 9633908979

22

Half Subtractor

 - Half subtractor is a combination circuit with two inputs and two outputs (difference and borrow).
- It produces the difference between the two binary bits at the input and also produces an output (Borrow) to indicate if a 1 has been borrowed.
- In the subtraction (A-B), A is called as Minuend bit and B is called as Subtrahend bit



JIBIN EP, EKC TC MANJERI, 9633908979

23

HALF SUBTRACTOR

0-0=0, 0-1=1 WITH BORROW 1
1-0=1, 1-1=0

TRUTH TABLE

Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

BOOLEAN EXPRESSION

For Difference

A \ B	0	1
0	0	1
1	1	0


$$\text{Difference} = AB + \bar{A}\bar{B} \\ = A \oplus B$$

For Borrow

A \ B	0	1
0	0	1
1	0	0

$$\text{Borrow} = \bar{A}B$$

LOGIC DIAGRAM

 


JIBIN EP, EKC TC MANJERI, 9633908979

24

Full Subtractor

 - The disadvantage of a half subtractor is overcome by full subtractor.
- The full subtractor is a combinational circuit with three inputs A, B, B_{in} and two outputs D and B_{out} .
- The three inputs A, B and B_{in} , denote the Minuend, Subtrahend, and Previous Borrow, respectively. The two outputs, D and B_{out} represent the difference and output borrow, respectively.



JIBIN EP, EKC TC MANJERI, 9633908979

25

FULL SUBTRACTOR

0-0 = 0, 0-1 = 1 WITH BORROW 1
1-0 = 1, 1-1 = 0

TRUTH TABLE

Inputs			Outputs	
A	B	B_{in}	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

JIBIN EP, EKC TC MANJERI, 9633908979

26

FULL SUBTRACTOR

0-0 =0, 0-1 =1 WITH BORROW 1
1-0=1, 1-1=0

TRUTH TABLE

Inputs			Outputs	
A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

BOOLEAN EXPRESSION

	00	01	11	10
0				
1				

JIBIN EP, EKC TC MANJERI, 9633908979

27

FULL SUBTRACTOR

0-0 =0, 0-1 =1 WITH BORROW 1
1-0=1, 1-1=0

TRUTH TABLE

Inputs			Outputs	
A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

BOOLEAN EXPRESSION

	00	01	11	10
0				
1				

JIBIN EP, EKC TC MANJERI, 9633908979

28

FULL SUBTRACTOR

0-0=0, 0-1=1 WITH BORROW 1
1-0=1, 1-1=0

TRUTH TABLE

Inputs			Outputs	
A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

BOOLEAN EXPRESSION

For D

A \ B B _{in}	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$D = \bar{A}B\bar{B}_{in} + \bar{A}BB_{in} + AB\bar{B}_{in} + ABB_{in}$$

For B_{out}

A \ B B _{in}	00	01	11	10
0	0	1	1	1
1	0	0	1	0


$$B_{out} = \bar{A}B_{in} + \bar{A}B + BB_{in}$$

JIBIN EP, EKC TC MANJERI, 9633908979

29

Reference : 3 Input XOR Gate

Inputs			outputs
W	X	Y	Q = A ⊕ B ⊕ C
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


$$\text{Sum} = A \oplus B \oplus C_{in}$$

JIBIN EP, EKC TC MANJERI, 9633908979

30

FULL SUBTRACTOR

LOGIC DIAGRAM

 

Difference

$$B_{in} \oplus (A \oplus B)$$

Borrow

$$B_{out} = \bar{A}B_{in} + \bar{A}B + BB_{in}$$


JIBIN EP, EKC TC MANJERI, 9633908979

31

FULL SUBTRACTOR

LOGIC DIAGRAM

 Implementation of Full Subtractor Circuit using two Half Subtr



JIBIN EP, EKC TC MANJERI, 9633908979

32

MODULE 3 (TOPIC-4)

MULTIPLEXER AND DEMULTIPLEXER

<https://youtu.be/J8-fKhmlWu4>
https://youtu.be/Tt_cZOn2YBk  YouTube

JIBIN EP, EKC TC MANJERI, 9633908979

33


MULTIPLEXER (MUX)

- Multiplexer is a digital circuit that has multiple inputs and a single output.
- It is also known as Data Selector.
- The Selection of particular input line is controlled by set of **Selection lines**
- Normally there are 2^n Input lines and n Selection Lines Whose bit combination determines which input is selected
- Therefore Multiplexer is '**Many to One**' and it provides digital equivalent of an analog selector switch

JIBIN EP, EKC TC MANJERI, 9633908979

34

MULTIPLEXER (MUX)

 

JIBIN EP, EKC TC MANJERI, 9633908979

35

TYPES OF MULTIPLEXER

n Selection Lines
 2^n Input Lines
 1 Output Line

2 : 1 Mux

4 : 1 Mux


8 : 1 Mux

JIBIN EP, EKC TC MANJERI, 9633908979

36

2:1 MULTIPLEXER

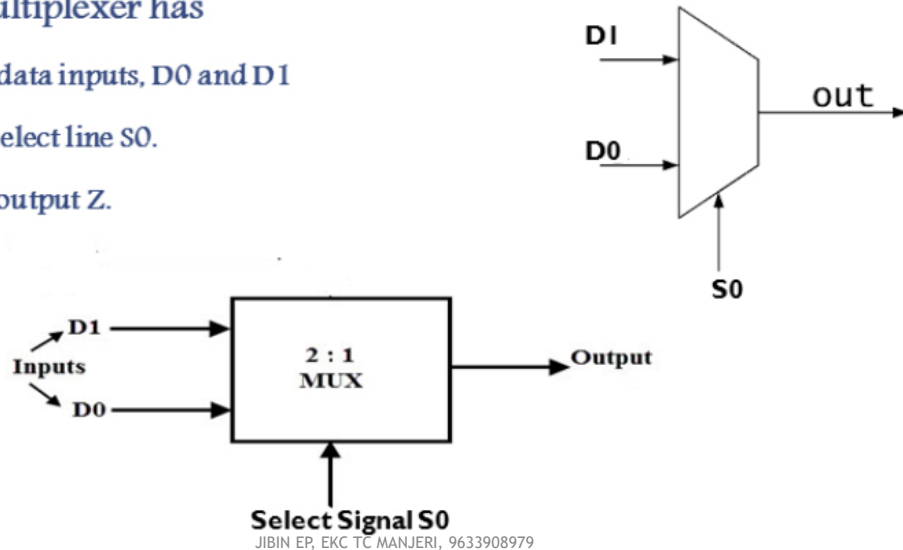
- 2:1 Multiplexer has
 - two data inputs, D0 and D1
 - one select line S0.
 - One output Z.



37

OPERATION OF 2:1 MUX

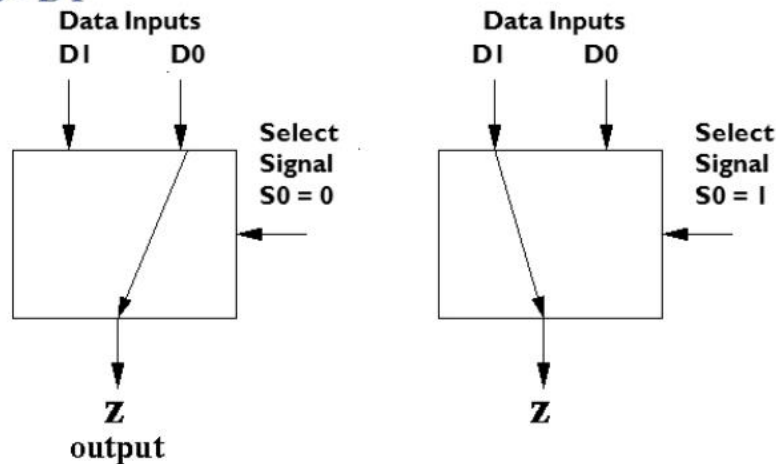- If Select Line $S_0=0$, then output = D0 and if Select Line $S_0=1$, then output = D1




38

2:1 MUX

S ₀	Output Z
0	D ₀
1	D ₁

$$Z = D_0 \cdot \overline{S_0} + D_1 \cdot S_0$$

Circuit

 



- 2:1 MUX requires
 - 2 AND Gates
 - 1 NOT Gate
 - 1 OR Gate

JIBIN EP, EKC TC MANJERI, 9633908979

39

4:1 MULTIPLEXER

  - 4:1 Multiplexer has
 - four data inputs, D₀, D₁, D₂ and D₃
 - Two select lines S₀ and S₁.
 - One output Z.



JIBIN EP, EKC TC MANJERI, 9633908979

40

TRUTH TABLE OF 4:1 MUX

S1	S0	Output Z
0	0	D0
0	1	D1
1	0	D2
1	1	D3


$$Z = D0.\overline{S1}.\overline{S0} + D1.\overline{S1}.S0 + D2.S1.\overline{S0} + D3.S1.S0$$

JIBIN EP, EKC TC MANJERI, 9633908979

41

CIRCUIT OF 4:1 MUX
 
$$Z = D0.\overline{S1}.\overline{S0} + D1.\overline{S1}.S0 + D2.S1.\overline{S0} + D3.S1.S0$$




JIBIN EP, EKC TC MANJERI, 9633908979

42

8:1 MULTIPLEXER

 - 8:1 Multiplexer has
 - Eight data inputs, D0, D1, D2, D3, D4, D5, D6 and D7
 - Three select lines S0, S1 and S2.
 - One output Z.



JIBIN EP, EKC TC MANJERI, 9633908979

43

TRUTH TABLE OF 8:1 MUX


S2	S1	S0	Output Z
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

$$Z = S2'.S1'.S0'.D0 + S2'.S1'.S0.D1 + S2'.S1.S0'.D2 + S2'.S1.S0.D3 + S2.S1'.S0'.D4 + S2.S1'.S0.D5 + S2.S1.S0'.D6 + S2.S1.S0.D7$$

JIBIN EP, EKC TC MANJERI, 9633908979

44

CIRCUIT OF 8:1 MUX

 

JIBIN EP, EKC TC MANJERI, 9633908979

45


DEMULTIPLEXER (DEMUX)

- Demultiplexer is a digital circuit that has multiple Outputs and a single Input.
- It is also known as Data Distributer
- The Section of particular Output line is controlled by set of Selection lines
- Normlly there are 2^n Output lines and n Selection Lines Whose bit combination determines which input is selected
- Therefore demultiplexer is 'One to Many'

JIBIN EP, EKC TC MANJERI, 9633908979

46

DEMULTIPLEXER (DEMUX)

 

JIBIN EP, EKC TC MANJERI, 9633908979

47

TYPES OF DEMULTIPLEXER

n Selection Lines
 2^n Output Lines
 1 Input Line

1:2 Mux

1:4 Mux

1:8 Mux

JIBIN EP, EKC TC MANJERI, 9633908979

48

1 x2 DEMUX



It has **one select line** and **two outputs**, Y_0 and Y_1 . The input connected is F.

TRUTH TABLE:

S_0	Y_0	Y_1
0	F	0
1	0	F

$$Y_0 = \overline{S_0} \cdot F + S_0 \cdot 0 = \overline{S_0} \cdot F$$
  
$$Y_1 = \overline{S_0} \cdot 0 + S_0 \cdot F = S_0 \cdot F$$



JIBIN EP, EKC TC MANJERI, 9633908979

Circuit


49

1 x4 DEMUX

It has **two select lines** and **four outputs**, Y_0 , Y_1 , Y_2 and Y_3 . The input connected is F.

TRUTH TABLE:

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	F	0	0	0
0	1	0	F	0	0
1	0	0	0	F	0
1	1	0	0	0	F

 

$$Y_0 = \overline{S_1} \cdot \overline{S_0} \cdot F$$

$$Y_1 = \overline{S_1} \cdot S_0 \cdot F$$


$$Y_2 = S_1 \cdot \overline{S_0} \cdot F$$

$$Y_3 = S_1 \cdot S_0 \cdot F$$


JIBIN EP, EKC TC MANJERI, 9633908979

50

1 x4 DEMUX CIRCUIT

 


51

 

52

APPLICATION OF DEMUX

 

JIBIN EP, EKC TC MANJERI, 9633908979

53

MODULE 3 (TOPIC-5)

MULTIPLEXER AND DEMULTIPLEXER (NUMERICAL PROBLEMS)

<https://youtu.be/2p9Ex6YPBc4>  YouTube

JIBIN EP, EKC TC MANJERI, 9633908979


54

Problem 1:

Implement the following function using 8-to-1 Mux

$$f(x,y,z) = \sum m(0,2,3,5)$$

S2	S1	S0	F
x	y	z	
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

JIBIN EP, EKC TC MANJERI, 9633908979

55

Problem 2:

Use a 4:1 Mux to implement the logic function

$$f(A,B,C) = \sum m(1,2,4,7)$$

Minterm	S2	S1	C	F	
	A	B			
0	0	0	0	0	F=C
1	0	0	1	1	
2	0	1	0	1	F=C'
3	0	1	1	0	
4	1	0	0	1	F=C'
5	1	0	1	0	
6	1	1	0	0	F=C
7	1	1	1	1	

JIBIN EP, EKC TC MANJERI, 9633908979


56

Problem 3a:

Use a multiplexer having Four data select the input to implement the logic for the function given below. Also realize the same using 16:1 Mux and 8:1 Mux

$$f = \sum m(0,1,2,3,4,10,11,14,15)$$

Minterm	S3 A	S2 B	S1 C	S0 D	F
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

 

JIBIN EP, EKC TC MANJERI, 9633908979

57

Problem 3b:

Use a multiplexer having three data select the input to implement the logic for the function given below. Also realize the same using 8:1 Mux

$$f = \sum m(0,1,2,3,4,10,11,14,15)$$

Minterm	S3 x	S2 x	S1 y	D	F
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

F=1

F=1

F=D'


F=0

F=0

F=1

F=0

F=1

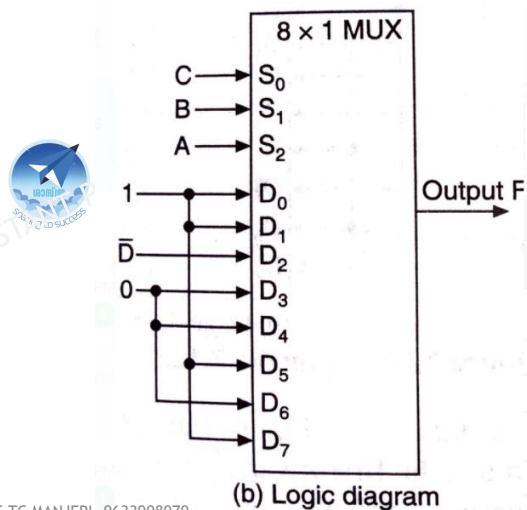


(b) Logic diagram

JIBIN EP, EKC TC MANJERI, 9633908979

58

 Problem 4

Use a demultiplexer Implement the functions $f_1 = \sum m(0,3,7)$ $f_2 = \sum m(1,2,5)$



JIBIN EP, EKC TC MANJERI, 9633908979

59

Problem 5 (Home Work)

Use Multiplexer implement the logic functions

$$F = A \oplus B \oplus C$$

Inputs			outputs
W	X	Y	$Q = A \oplus B \oplus C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



JIBIN EP, EKC TC MANJERI, 9633908979

60

Problem 6 (Home Work)

Use a demultiplexer Implement the functions $f_1 = \sum m(1,5,7)$ $f_2 = \sum m(3,6,7)$

**Problem 7 (Home Work)**

Implement the functions $f(w,x,y,z) = \sum m(1,4,6,7,8,9,10,11,15)$ Using 8 to 1 Mux



MODULE 3 (TOPIC-6)

DECODER AND ENCODER


<https://youtu.be/Zxd-imLGFr>  YouTube

JIBIN EP, EKC TC MANJERI, 9633908979

63

DECODER

 - Decoder is a Multiple Input , Multiple Output logic circuit which converts coded inputs to coded outputs, where the input and output are different
- Decoder consist of n input and 2^n Maximum Possible Outputs



JIBIN EP, EKC TC MANJERI, 9633908979

64

Examples

2 to 4

3 to 8


4 to 16

JIBIN EP, EKC TC MANJERI, 9633908979

65

Binary Decoder (2 to 4 Decoder)


Inputs			Outputs			
ENABLE	A	B	Y3	Y2	Y1	Y0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 

JIBIN EP, EKC TC MANJERI, 9633908979

66

3 to 8 Decoder

 

JIBIN EP, EKC TC MANJERI, 9633908979

67


3 to 8 Decoder

Inputs				Outputs							
ENABLE	A	B	C	Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

JIBIN EP, EKC TC MANJERI, 9633908979

68

 Implement the Boolean function $f = \sum m(1,2,3,7)$




JIBIN EP, EKC TC MANJERI, 9633908979

69

ENCODER

 - Encoder is a digital circuit which perform inverse operation of Decoder
- Decoder is a Multiple Input , Multiple Output logic circuit which converts coded inputs to coded outputs, where the input and output are different
- Decoder consist of n Outputs and 2^n Maximum Possible Inputs



JIBIN EP, EKC TC MANJERI, 9633908979

70

Examples



JIBIN EP, EKC TC MANJERI, 9633908979

71


8 TO 3 ENCODER (OCTAL TO BINARY)

Inputs								Outputs		
D0	D1	D2	D3	D4	D5	D6	D7	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

JIBIN EP, EKC TC MANJERI, 9633908979

72

8 TO 3 ENCODER (OCTAL TO BINARY)

 

JIBIN EP, EKC TC MANJERI, 9633908979

73



PRIORITY ENCODER

- A Priority encoder is one of the types of encoders in which an ordering is imposed to the inputs that means compared with the standard encoder, it includes the **priority function**.
- However, this priority is based on the relative magnitudes of the inputs. Hence, the input with larger magnitude is the one that is encoded first.
- Priority encoders can select the inputs with highest priority in many practical applications. This process of selection is called **arbitration**.
- One of the most common examples of arbitration is that, there are numerous input devices in computer system and several of which devices attempt to supply the data to the computer simultaneously. In those cases, a priority encoder enables the input device having the highest priority among those devices trying to access the computer at the same time.

JIBIN EP, EKC TC MANJERI, 9633908979

74



PRIORITY ENCODER

This Priority encoder consists of 4 inputs and three outputs.

Although an encoder has 2^n inputs and n outputs, it has a third output 'V' which is a valid bit indicator and is set to one when one or more inputs are active or equal to 1.

$$Y_1 = D_3 + \overline{D_3} D_2 = D_3 + D_2$$

$$Y_0 = D_3 + \overline{D_3} \overline{D_2} D_1 = D_3 + \overline{D_2} D_1$$

$$V = D_3 + D_2 + D_1 + D_0$$


Inputs				Outputs		
D_0	D_1	D_2	D_3	Y_1	Y_0	V
0	0	0	0	×	×	0
1	0	0	0	0	0	1
×	1	0	0	0	1	1
×	×	1	0	1	0	1
×	×	×	1	1	1	1

JIBIN EP, EKC TC MANJERI, 9633908979

75



PRIORITY ENCODER

 

JIBIN EP, EKC TC MANJERI, 9633908979

76

MODULE 3 (TOPIC-7)

MAGNITUDE COMPARATORS

<https://youtu.be/7xHM5HeGChg>




JIBIN EP, EKC TC MANJERI, 9633908979

77

MAGNITUDE COMPARATOR

- A magnitude digital comparator is a combinational circuit that compares two digital or binary numbers (consider A and B) and determines their relative magnitudes in order to find out whether one number is equal, less than or greater than the other digital number.
- Three binary variables are used to indicate the outcome of the comparison as $A > B$, $A < B$, or $A = B$. The below figure shows the block diagram of a n-bit comparator which compares the two numbers of n-bit length and generates their relation between themselves.

 

JIBIN EP, EKC TC MANJERI, 9633908979

78

Single Bit Magnitude Comparator

- comparator used to compare two bits, i.e., two numbers each of single bit is called a single bit comparator. It consists of two inputs for allowing two single bit numbers and three outputs to generate less than, equal and greater than comparison outputs.
- The figure below shows the block diagram of a single bit magnitude comparator. This comparator compares the two bits and produces one of the 3 outputs as L ($A < B$), E ($A = B$) and G ($A > B$).




JIBIN EP, EKC TC MANJERI, 9633908979

79

Truth Table

A_0	B_0	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 


JIBIN EP, EKC TC MANJERI, 9633908979

80

Two Bit Magnitude Comparator

- A 2-bit comparator compares two binary numbers, each of two bits and produces their relation such as one number is equal or greater than or less than the other. The figure below shows the block diagram of a two-bit comparator which has four inputs and three outputs.
- The first number A is designated as $A = A_1A_0$ and the second number is designated as $B = B_1B_0$. This comparator produces three outputs as $G = 1$ if $A > B$.

 

JIBIN EP, EKC TC MANJERI, 9633908979

81

Inputs				Outputs		
A ₁	A ₀	B ₁	B ₀	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

JIBIN EP, EKC TC MANJERI, 9633908979

		A > B			
A ₁ A ₀	B ₁ B ₀	00	01	11	10
		0	0	0	0
01		1	0	0	0
11		1	1	0	1
10		1	1	0	0

		A = B			
A ₁ A ₀	B ₁ B ₀	00	01	11	10
		1	0	0	0
01		0	1	0	0
11		0	0	1	0
10		0	0	0	1

82



$$A > B: G = A_0 \overline{B_1} \overline{B_0} + A_1 \overline{B_1} + A_1 A_0 \overline{B_0}$$

$$A = B: E = \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 A_0 B_1 B_0 + A_1 \overline{A_0} B_1 \overline{B_0}$$

$$= \overline{A_1} \overline{B_1} (\overline{A_0} \overline{B_0} + A_0 B_0) + A_1 B_1 (A_0 B_0 + \overline{A_0} \overline{B_0})$$


$$= (A_0 B_0 + \overline{A_0} \overline{B_0}) (A_1 B_1 + \overline{A_1} \overline{B_1})$$

$$= (A_0 \text{ Ex-NOR } B_0) (A_1 \text{ Ex-NOR } B_1)$$

$$A < B: L = \overline{A_1} B_1 + \overline{A_0} B_1 B_0 + \overline{A_1} \overline{A_0} B_0$$

JIBIN EP, EKC TC MANJERI, 9633908979

83

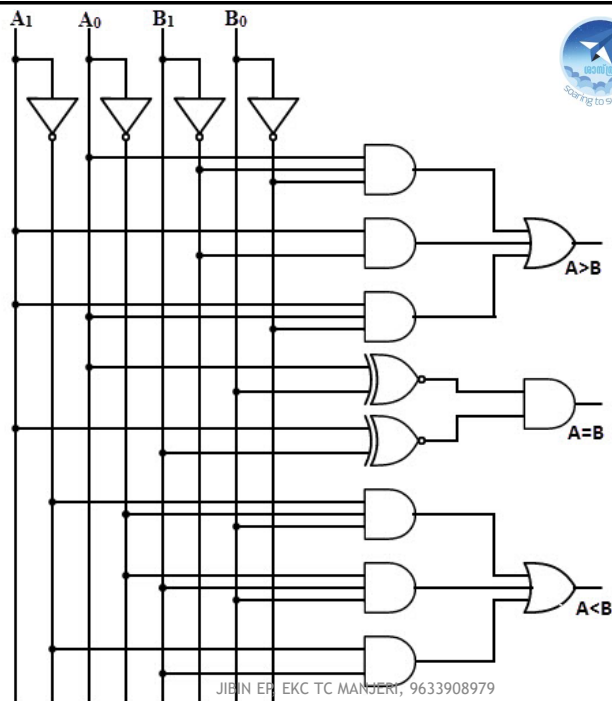

JIBIN EP, EKC TC MANJERI, 9633908979

84

Application of Comparators



- These are used in the address decoding circuitry in computers and microprocessor based devices to select a specific input/output device for the storage of data.
- These are used in control applications in which the binary numbers representing physical variables such as temperature, position, etc. are compared with a reference value. Then the outputs from the comparator are used to drive the actuators so as to make the physical variables closest to the set or reference value.
- Process controllers
- Servo-motor control

JIBIN EP, EKC TC MANJERI, 9633908979

85

MODULE 3 (TOPIC-9)

BINARY PARALLEL ADDER CARRY LOOK AHEAD ADDER BCD ADDER

https://youtu.be/8G29L4BFg_o
<https://youtu.be/hfbvmGZ79SA>



JIBIN EP, EKC TC MANJERI, 9633908979

86



PARALLEL ADDER


- A single full adder performs the addition of two one bit numbers and an input carry.
- But a **Parallel Adder** is a digital circuit capable of finding the arithmetic **sum** of two binary numbers that is **greater than one bit** in length by operating on corresponding pairs of bits in parallel.
- It consists of **full adders connected in a chain** where the output carry from each full adder is connected to the carry input of the next higher order full adder in the chain.
- **A n bit parallel adder requires n full adders to perform the operation.** So for the two-bit number, two adders are needed while for four bit number, four adders are needed and so on. Parallel adders normally incorporate carry lookahead logic to ensure that carry propagation between subsequent stages of addition does not limit addition speed.

JIBIN EP, EKC TC MANJERI, 9633908979

87



PARALLEL ADDER

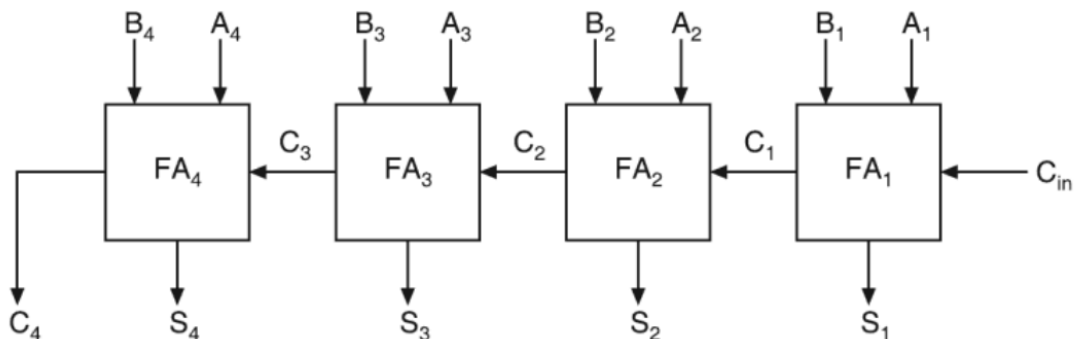

JIBIN EP, EKC TC MANJERI, 9633908979

88



CARRY LOOK AHEAD ADDER

- A carry-Lookahead adder is a fast parallel adder as it reduces the propagation delay by more complex hardware, hence it is costlier. In this design, the carry logic over fixed groups of bits of the adder is reduced to two-level logic, which is nothing but a transformation of the ripple carry design.
- This method makes use of logic gates so as to look at the lower order bits of the augend and addend to see whether a higher order carry is to be generated or not.
- **Carry-Lookahead Adder Ics** A typical carry-Lookahead generator IC is 74182 which accept four pairs of active low carry propagate (as P0, P1, P2 and P3) and carry generate (Go, G1, G2 and G3) signals and an active high input (Cn).

JIBIN EP, EKC TC MANJERI, 9633908979

89



CARRY LOOK AHEAD ADDER

Consider the full adder circuit shown above with corresponding truth table. If we define two variables as carry generate G_i and carry propagate P_i then,

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

The sum output and carry output can be expressed as


$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

A	B	C_i	C_{i+1}	Condition
0	0	0	0	No carry generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No carry propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	Carry generate
1	1	1	1	


JIBIN EP, EKC TC MANJERI, 9633908979

90

 

JIBIN EP, EKC TC MANJERI, 9633908979

91

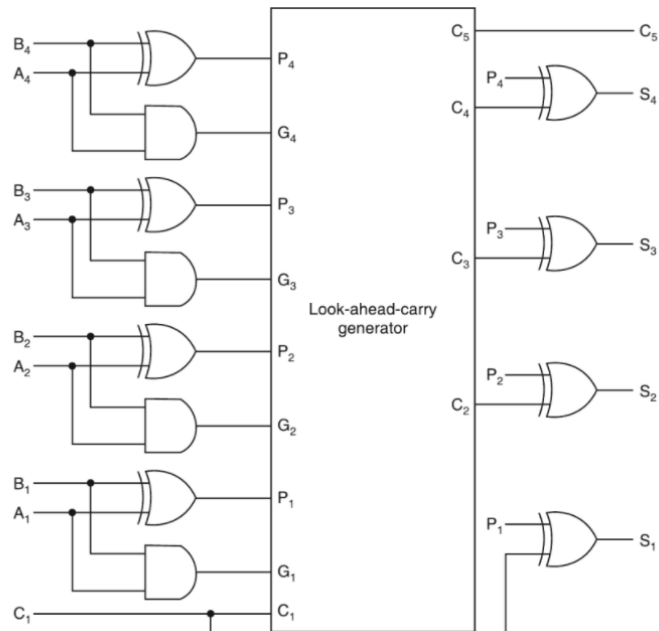

JIBIN EP, EKC TC MANJERI, 9633908979

92



BCD ADDER


- BCD adder must be able to operate in accordance with above steps
- 1) Add two bit BCD Code Groups , using straight binary addition
- 2) Determine if the sum of addition is greater than 1001 (Decimal 9); If it is , add 0110 (Decimal 6) to this sum and generate a carry to the next decimal position
- The first requirement is easily met by using a 4 bit binary parallel adder
- The sum output $S_4 S_3 S_2 S_1 S_0$ can range anywhere from 00000 to 10010

The Circuitry for a BCD adder must include the logic needed to detect whenever the sum is greater than 01001, so that correction can be added in

The circuit consists of three basic parts. The two BCD code groups $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$ are added together in the upper 4-bit adder, to produce the sum $S_4S_3S_2S_1S_0$. The logic gates shown implement the expression for X. The lower 4-bit adder will add the correction 0110 to the sum bits, only when $X = 1$, producing the final BCD sum output represented by $\Sigma_3\Sigma_2\Sigma_1\Sigma_0$. The X is also the carry-out that is produced when the sum is greater than 01001. Of course, when $X = 0$, there is no carry and no addition of 0110. In such cases, $\Sigma_3\Sigma_2\Sigma_1\Sigma_0 = S_3S_2S_1S_0$.

Two or more BCD adders can be connected in cascade when two or more digit decimal numbers are to be added. The carry-out of the first BCD adder is connected as the carry-in of the second BCD adder, the carry-out of the second BCD adder is connected as the carry-in of the third BCD adder and so on.

- - - -

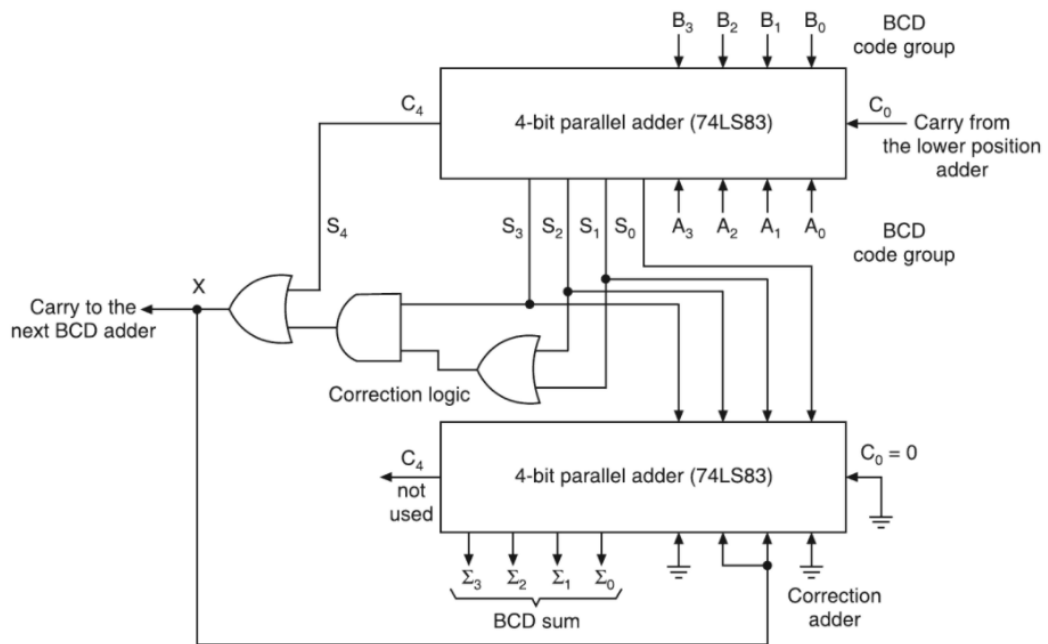

95

MODULE 3 (TOPIC-9)


VERILOG PROGRAMMING PART 2

<https://youtu.be/ZgGDLuHmpOE>  YouTube

JIBIN EP, EKC TC MANJERI, 9633908979


96

2:1 MUX

 

2:1 Mux Theory

Circuit Diagram

 

$$Y = D0.S' + D1.S$$

Truth Table

S	Y
0	D0
1	D1

2:1 MODELING DATA FLOW MODELING

Boolean Expression


$$Y = D0.S' + D1.S$$

```

module 2TO1MUX(D0, D1, S, Y);
output Y;
Input D0, D1, S;
assign Y = (D0~S) | (D1S);
end module

```

2:1 MODELING GATE LEVEL MODELING

 


```

module 2TO1MUX(Y, D0, D1, S);
output Y;
input D0, D1, S;
wire T1, T2, Sbar;
and (T1, D1, S), (T2, D0, Sbar);
not (Sbar, S);
or (Y, T1, T2);
endmodule


```

4:1 MUX

 

4:1 Mux Theory

Circuit Diagram

 

Truth Table

S0	S1	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

Boolean


$$Y = D0S0'S1' + D1.S0'S1 + D2S0S1' + D3S0S1$$

4:1 MODELING GATE LEVEL MODELING


```

module 4TO1 MUX(out, a, b, c, d, s0,
s1); output out;
input a, b, c, d, s0, s1;
wire sobar, s1bar, T1, T2, T3, T4;
not (s0bar, s0), (s1bar, s1);
and (T1, a, s0bar, s1bar), (T2, b, s0bar,
s1), (T3, c, s0, s1bar), (T4, d, s0, s1);
or(out, T1, T2, T3, T4);
endmodule

```

 

TYPES OF COMBINATIONAL CIRCUITS

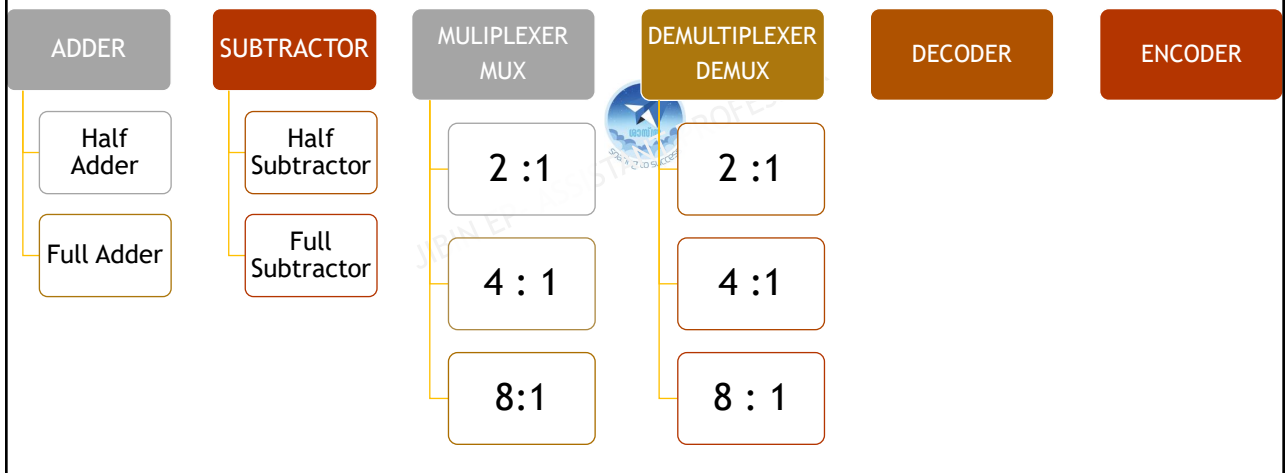

HALF ADDER

$0+0=0, 0+1=1$
 $1+0=1, 1+1=0$

TRUTH TABLE

Inputs		Outputs	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

BOOLEAN EXPRESSION

For Carry

A \ B	0	1
0	0	0
1	0	1


$$\text{Carry} = AB$$

For Sum

A \ B	0	1
0	0	1
1	1	0


$$\begin{aligned}\text{Sum} &= A\bar{B} + \bar{A}B \\ &= A \oplus B\end{aligned}$$

LOGIC DIAGRAM

 

HALF ADDER GATE LEVEL MODELING

Refer the Video

 



FULL ADDER

0+0 =0, 0+1 =1
1+0=1, 1+1= 0

TRUTH TABLE


Inputs			Outputs	
A	B	C _{in}	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

BOOLEAN EXPRESSION

  

FULL ADDER

LOGIC DIAGRAM

 

Refer the Video

$$Sum = A \oplus B \oplus C_{in}$$

$$Carry = AB + AC_{in} + BC_{in}$$

HALF SUBTRACTOR

TRUTH TABLE

Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

BOOLEAN EXPRESSION

For Difference

A \ B	0	1
0	0	1
1	1	0


$$\text{Difference} = A\bar{B} + \bar{A}B \\ = A \oplus B$$

For Borrow

A \ B	0	1
0	0	1
1	0	0


$$\text{Borrow} = \bar{A}B$$

LOGIC DIAGRAM

 

HALF SUBTRACTOR

LOGIC DIAGRAM

 

Refer the Video

PREPARED BY



Jibin EP

SHAstra TECHNICAL INSTITUTE

KTU | PSC | UPSC



Jibin EP

Assistant Professor
Department of Electronics and Communication
Ernad Knowledge City Technical Campus Manjeri
Contact : 9633908979, 70121716607
Email : epjibin@gmail.com, jibin@ekc.edu.in



<https://www.youtube.com/ShastraTechnicalInstitute>

113